



Lab Report

LAB — 04

CSE — 206

Presented By:

- **Name:** Tunazzinur Rahman Kabbo
- **Intake:** 44
- **Sec:** 07
- **ID:** 19202103268

CSE — 206

Presented To:

❖ **Iffat Tamanna**

Lecturer, BUBT

Department of Computer Science & Engineering

Email: iffat@bubt.edu.bd

LAB-04

Name of the experiment: Construct and test various adder and subtractor circuits.

Description:

Adder: An adder is a digital circuit that performs addition of numbers. Adders are two types : (i) Half adder
(ii) Full adder

(i) Half Adder: A half adder is a type of adder, that is able to add two binary digits and provide the output plus a carry value. It has two inputs and two outputs. The common representation uses a XOR logic gate and an AND logic gate.

$$\therefore \text{Carry (C)} = XY$$

$$\therefore \text{Sum (S)} = X'Y + XY' = X \oplus Y$$


Truth Table:

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Equipments:

- (i) LOGICSTATE
- (ii) LOGICPROBE
- (iii) XOR Gate
- (iv) AND Gate

Half Adder

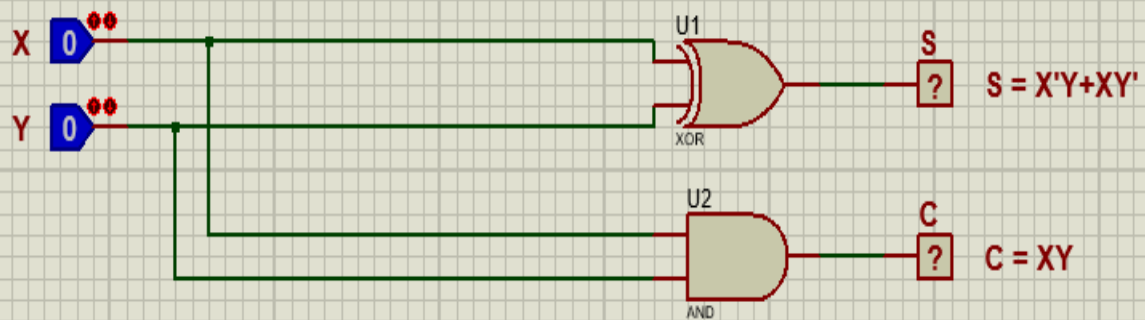

Full Adder: A full adder circuit is central to most digital circuits that perform addition. It is so called because it adds together two binary digits, plus a carry in digit to produce a sum and carry out digit. It has three inputs and two outputs.

$$\therefore \text{Carry } (C) = XY + XZ + YZ$$

$$\therefore \text{Sum } (S) = X'Y'Z + X'YZ' + XY'Z' + XYZ$$

It can also be written with two half adders

$$\text{Then, Carry, } (C) = XY + Z(X+Y)$$

$$\text{Sum, } (S) = Z \oplus (X \oplus Y)$$

Truth Table:

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Equipments:



Normal Full Adder:

- (i) LOGIC PROBE
- (ii) LOGIC STATE
- (iii) 3 input AND Gate
- (iv) 4 input OR Gate
- (v) 3 input OR Gate
- (vi) 2 input AND Gate


Full Adder with half adder:

- (i) LOGIC PROBE
- (ii) LOGIC STATE
- (iii) XOR Gate
- (iv) AND Gate
- (v) OR Gate

Normal Full Adder

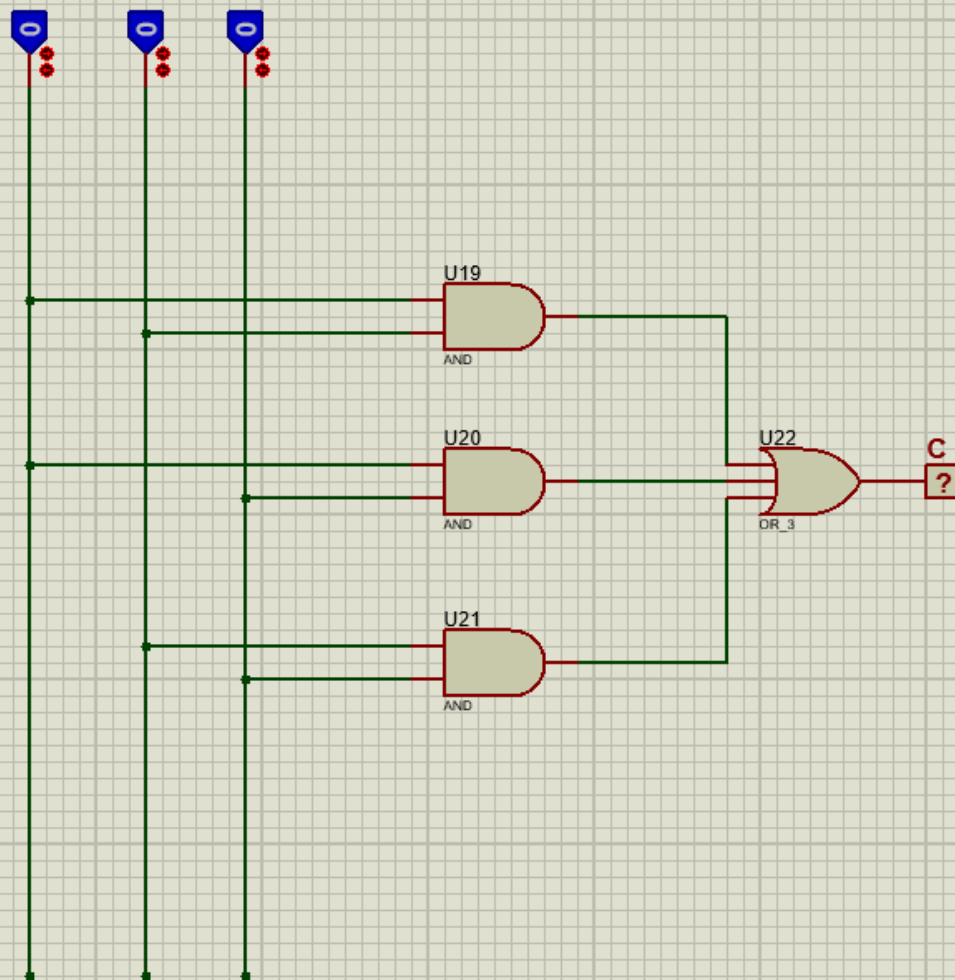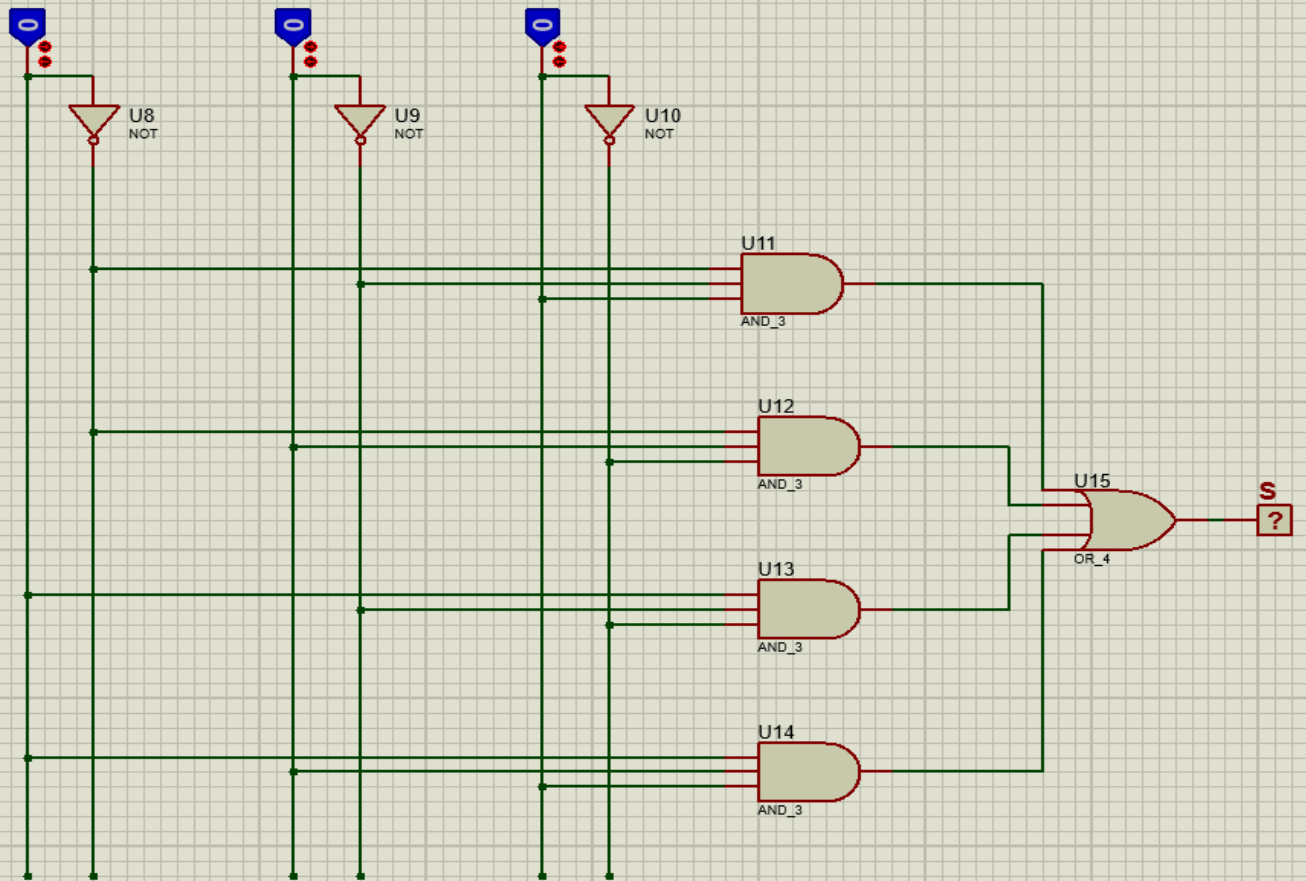

Full adder with two half adders

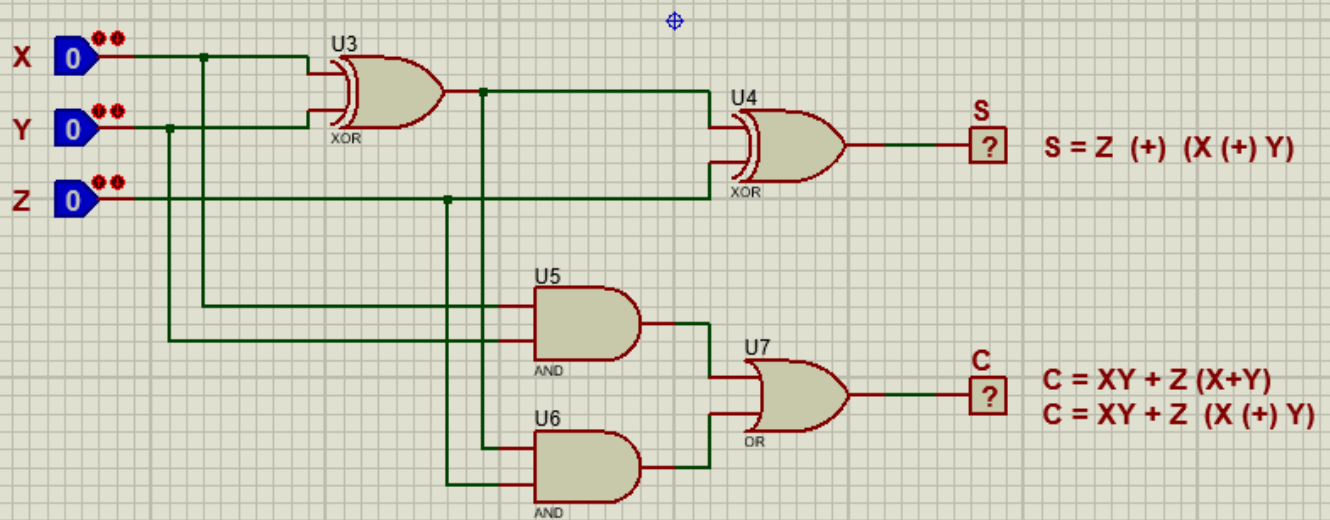

Subtractor: Subtractor circuits take two binary numbers as input and subtract one number from another. It gives two outputs. (Difference and Borrow).

There are two types of subtractor:

- (i) Half Subtractor
- (ii) Full Subtractor

(i) Half Subtractor: The half subtractor is a combinational circuit which is used to perform subtraction of two bits. It has two inputs and two outputs. It doesn't consider the previous borrow.

$$\therefore \text{Borrow (B)} = X'Y$$

$$\therefore \text{Difference (D)} = X'Y + XY'$$

$$= X \oplus Y$$

= Adder's Sum


Truth Table:

X	Y	B	D
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

Equipments:

- (i) LOGIC STATE
- (ii) LOGIC PROBE
- (iii) XOR Gate
- (iv) NOT Gate
- (v) AND Gate.

Half Subtractor

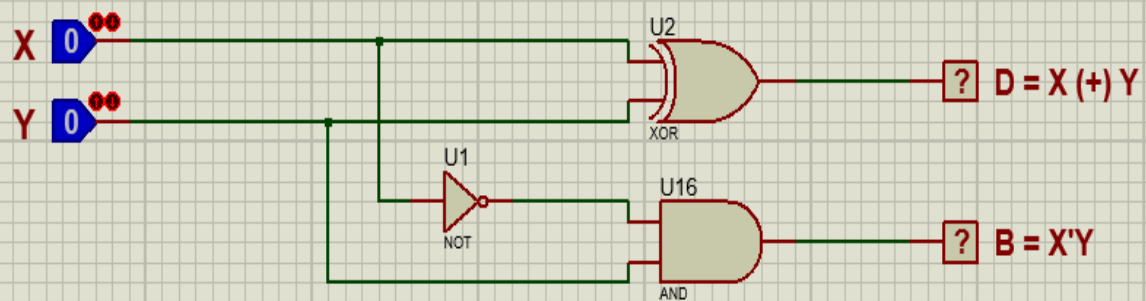

Full Subtractor: A full subtractor performs subtraction involving three bits (X, Y, Z) . Here (X, Y) are literal and Z is previous borrow. It has three inputs and two outputs. It considers the previous borrow.

$$\therefore \text{Borrow, } (B) = X'Z + X'Y + YZ$$

$$\begin{aligned}\therefore \text{Difference } (D) &= X'Y'Z + X'YZ' + XY'Z' + XY'Z + XYZ \\ &= \text{Sum of full adder.}\end{aligned}$$

\therefore It can also be written with two half subtractors.

Then,

$$\begin{aligned}\text{Borrow, } (B) &= \bar{X}Y + Z(\overline{X \oplus Y}) \\ \text{Difference, } (D) &= Z \oplus (X \oplus Y)\end{aligned}$$

Truth Table;

X	Y	Z	B	D
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Equipments:



Normal Full Subtractor

- (i) LOGICPROBE
- (ii) LOGICSTATE
- (iii) AND Gate
- (iv) NOT Gate
- (v) 3 input OR Gate


Full Subtractor with two half subtractor

- (i) LOGICSTATE
- (ii) LOGICPROBE
- (iii) XOR Gate
- (iv) NOT Gate
- (v) AND Gate
- (vi) OR Gate

Normal Full Subtractor

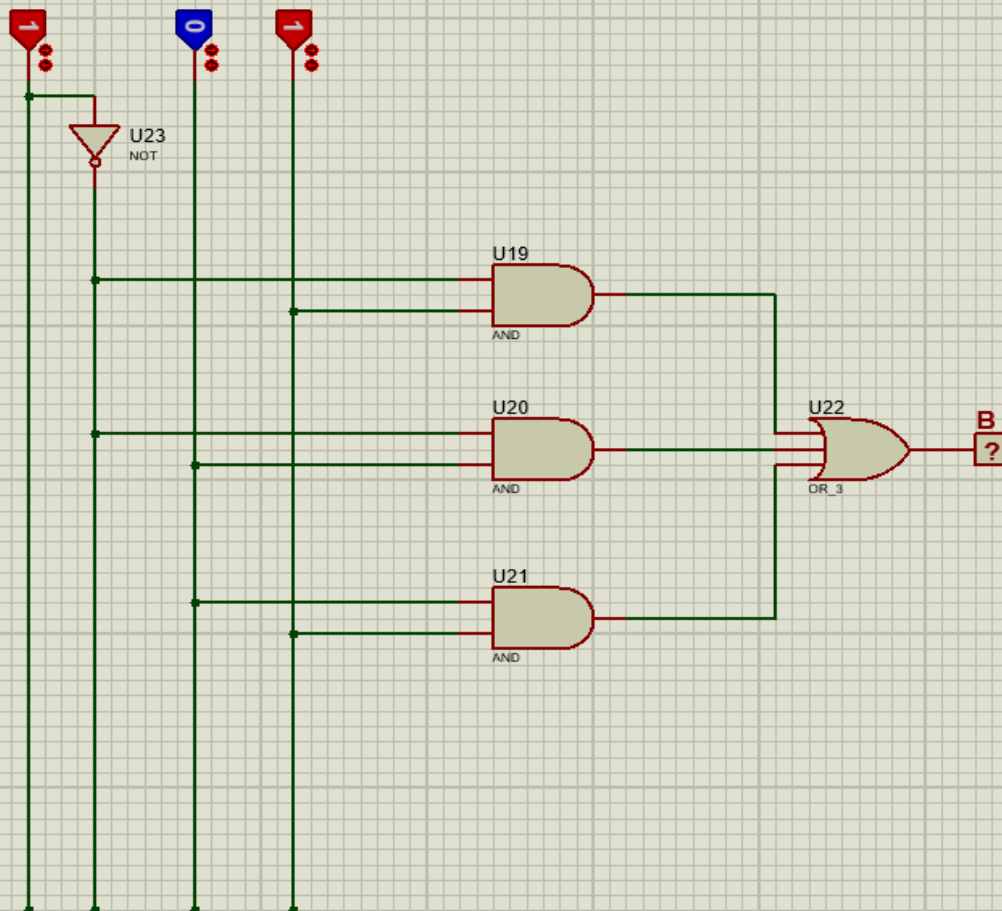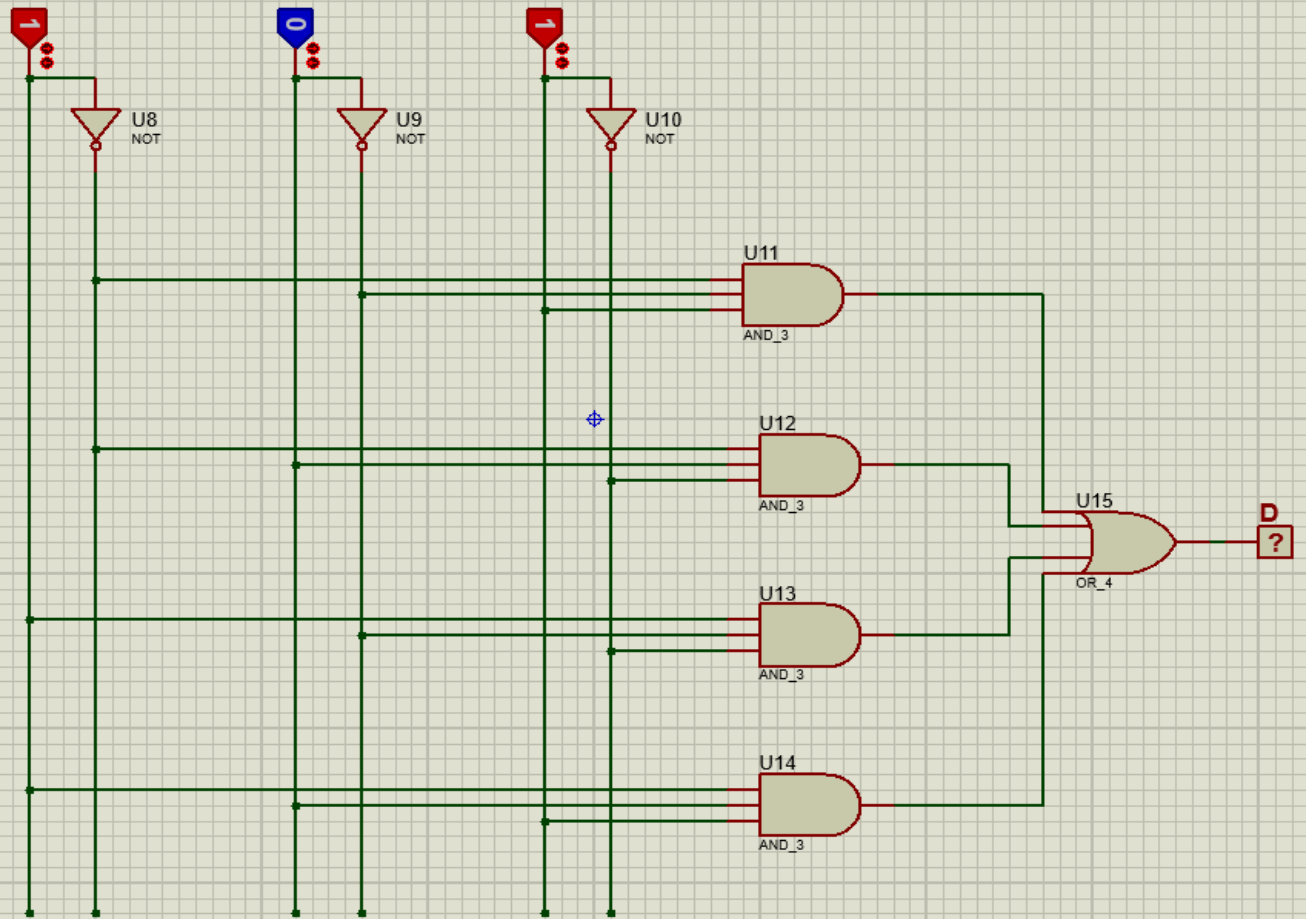

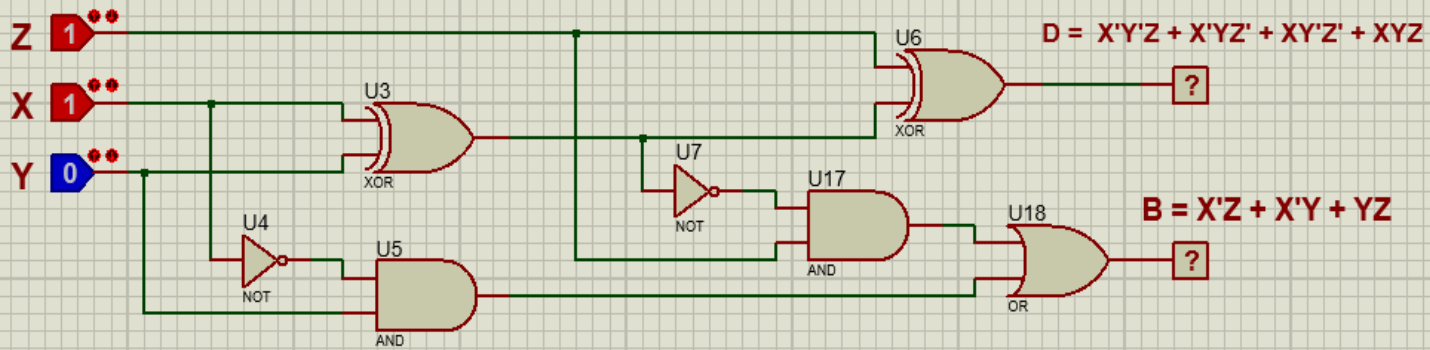Full subtractor with two half subtractors



Conclusion;

- (i) We learnt how to implement Adder circuit.
- (ii) We learnt how to implement Subtractor circuit.
- (iii) We learnt how to add two binary bits and find out carry and sum.
- (iv) We learnt how to subtract two or three bits and find out Borrow and the Difference.
- (v) We learnt implementation of full adder using half adders.
- (vi) We learnt implementation of full subtractor using half subtractors.

THE END