

### **Lab Report**

LAB — 09

**CSE - 206** 

#### Presented By:

• Name: Tunazzinur Rahman Kabbo

• Intake: 44

• **Sec:** 07

• **ID**: 19202103268

#### **Presented To:**

Iffat Tamanna


Lecturer, BUBT
Department of Computer Science & Engineering
Email: iffat@bubt.edu.bd

### Lab-09


Mame of the experiment: Designing of 4-bit magnitude comparator using 741.585 Tc and full adder using decoders.
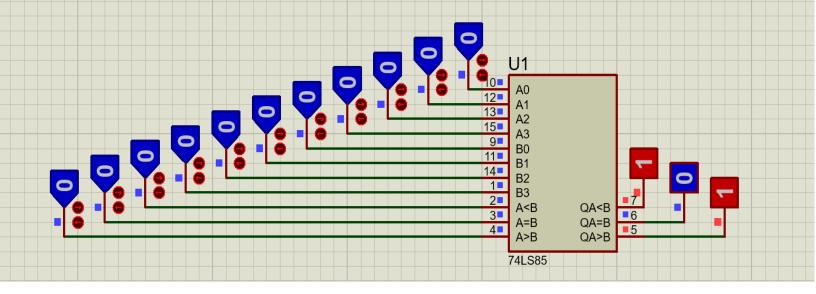
## Description:

A comparator that is used for comparing two binary numbers each of four bits are called a 4-bit magnitude comparator. It compares whether a binary number is equal less or greater. Than the other binary numbers. For building this or with logic gates we swill have two inputs (A and B) and have three outputs: one for A>B, another one for A<B and lastly for A=B condition.



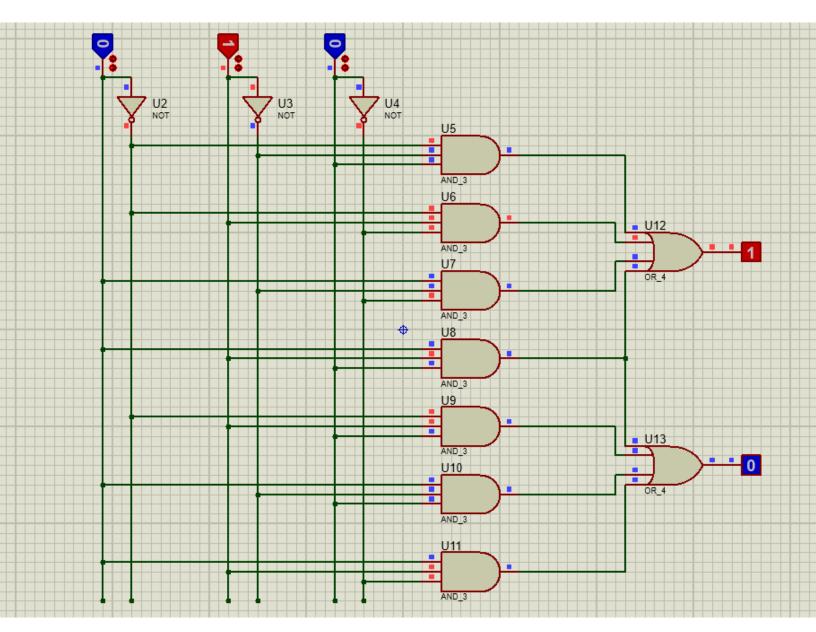4-bit Magnitude Comparator Using 74LS85 IC



Full Adder Using Decoder

# Condution:

- (i) We have learnt about magnitude comparcator.
  (ii) We have learnt about full adder and how to implement it with decoders.
- (iii) We have learnt how to implement a 4-bit magnitude comparator using 741585 To.

