



# Lab Report

**LAB — 05**

**CSE — 206**

## **Presented By:**

- **Name:** Tunazzinur Rahman Kabbo
- **Intake:** 44
- **Sec:** 07
- **ID:** 19202103268

CSE — 206

## **Presented To:**

❖ **Iffat Tamanna**

Lecturer, BUBT

Department of Computer Science & Engineering

Email: [iffat@bubt.edu.bd](mailto:iffat@bubt.edu.bd)

## Lab-05

Name of the experiment: Design, construct and test combination logic circuitry like parity generator.

Explanation:

A parity bit, or check bit, is a bit added to a string of binary code. Parity bits are a simple form of error detecting code. Parity bits are generally applied to the smallest units of a communication protocol, typically 8-bit octets, although they can also be applied separately to an entire message string of bits. The parity bit ensures that the total number of 1-bits in the string is even or odd. There are two variants of parity bits: even parity bit, odd parity bit.

Even parity: Here all the total number of bits in the message is made even.


Truth table:

A	B	C	P	Result
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

K-Map:

AB \ CP	00	01	11	10
00	0	1	0	1
01	1	0	1	0
11	0	1	0	1
10	1	0	1	0
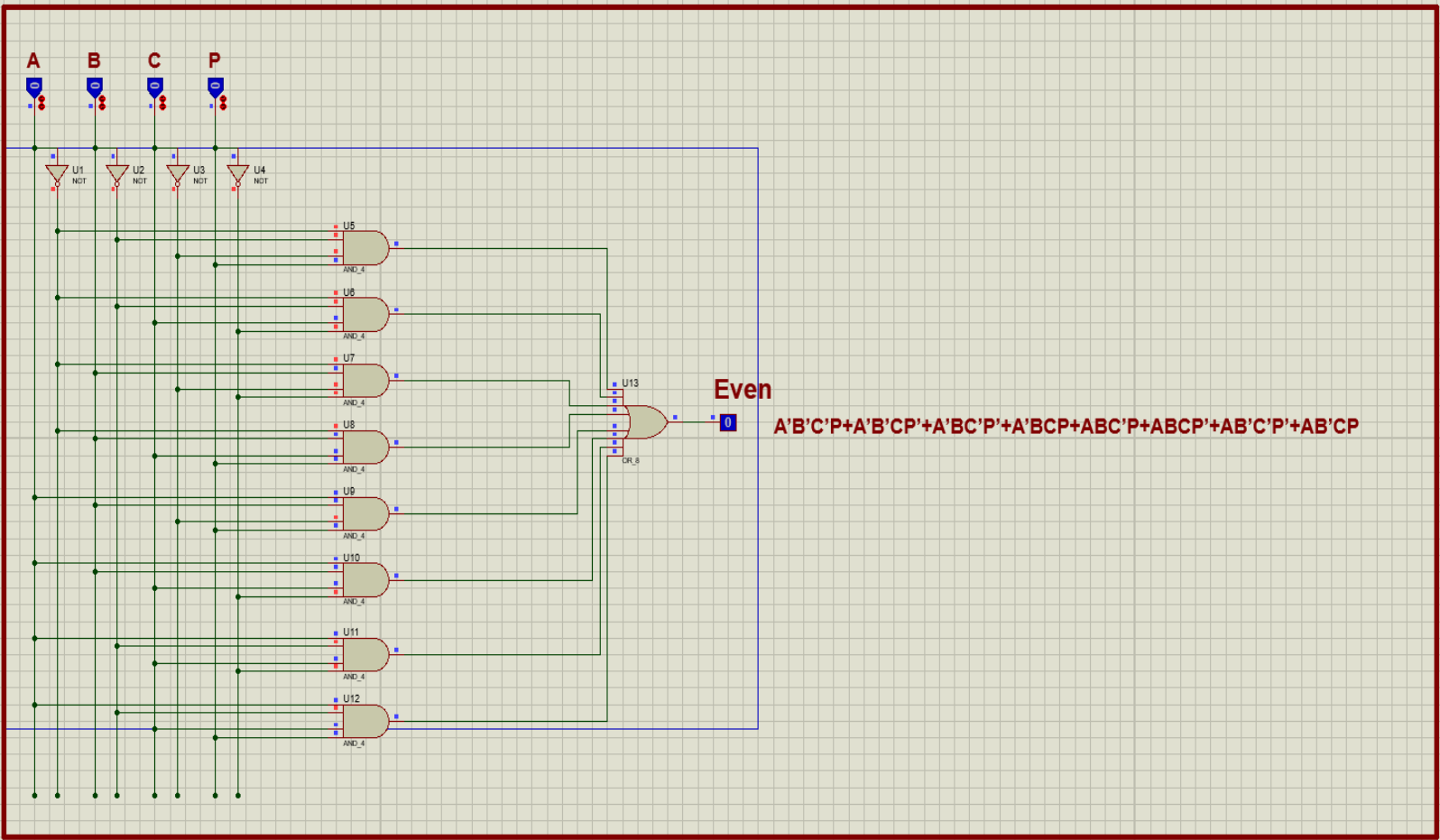
$$F = A'B'C'P + A'B'CP' + A'BC'P' + A'BCP + ABC'P + ABCP' + AB'C'P' + AB'CP$$



Odd parity: Hence the total number of bits in the message is made odd.


Truth table:

W	X	Y	P	Result
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

K-Map:

WX \ YP	00	01	11	10
00	1	0	1	0
01	0	1	0	1
11	1	0	1	0
10	0	1	0	1
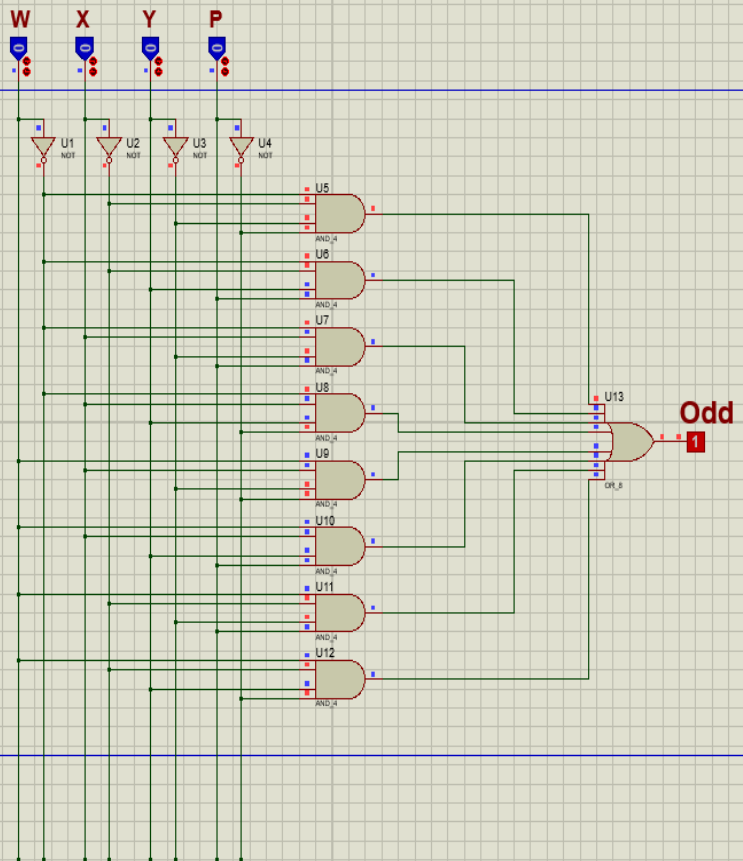
$$F = W'X'Y'P' + W'X'YP' + W'XY'P' + W'XYP' + WXY'P' + WXP + WX'Y'P' + WX'YP'$$



Odd

$$W'X'Y'P' + W'X'YP + W'XY'P' + W'XYP' + WXY'P' + WXP + WX'Y'P' + WX'YP'$$

Name of the experiment: Design of code converters like BCD to Excess-3

Description: Excess-3 binary code is an unweighted self-complementary BCD code. Self-complementary property means that the 1's complement of an excess-3 number is the excess-3 code of the 9's complement of the corresponding decimal number. This property is used since a decimal number can be nine's complement as easily as a binary number can be one's complemented; just by inverting all bits.

The process of converting BCD to excess-3 is quite simple from other conversions. The Excess-3 code can be calculated by adding 3 to each four digit BCD code.

Truth table:

Decimal	BCD				Excess-3			
	W	X	Y	P	A	B	C	D
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0
10	1	0	1	0	X	X	X	X
11	1	0	1	1	X	X	X	X
12	1	1	0	0	X	X	X	X
13	1	1	0	1	X	X	X	X
14	1	1	1	0	X	X	X	X
15	1	1	1	1	X	X	X	X

Now, we will use the K-map method to design the logical circuit for the conversion of BCD to Excess-3 code.



wx/yP	00	01	11	10
00	0	0	0	0
01	0	1	1	1
11	X	X	X	X
10	1	1	X	X

$$A = W + XP + XY$$

wx/yP	00	01	11	10
00	0	1	1	1
01	1	0	0	0
11	X	X	X	X
10	0	1	X	X


$$B = X'P + X'Y + XY'P'$$

wx/yP	00	01	11	10
00	1	0	1	0
01	1	0	1	0
11	X	X	X	X
10	1	0	X	X

$$C = Y'P' + YP$$

	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	X	X	X	X
10	1	0	X	X

$$D = P'$$

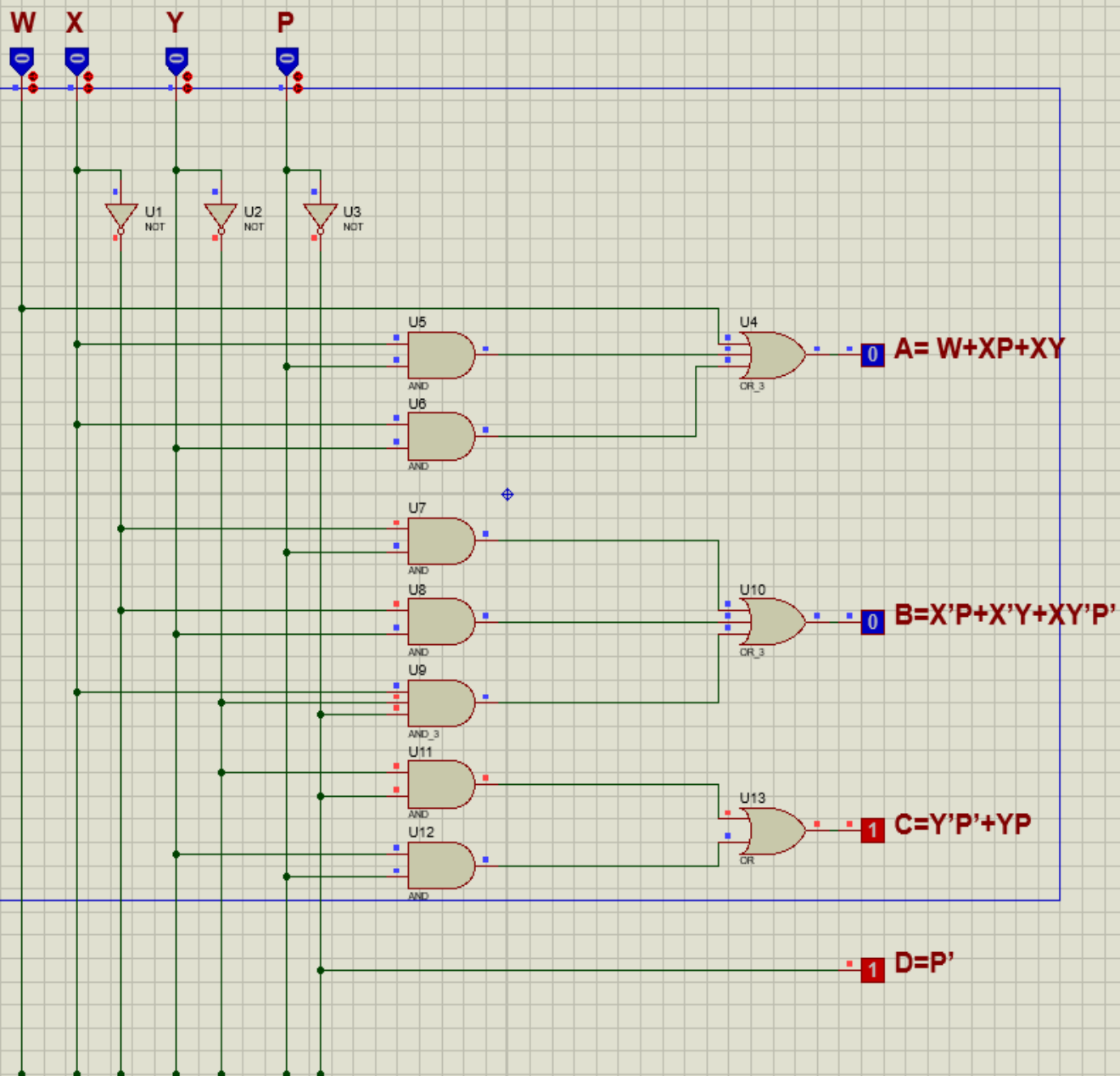

## Conclusion:

- (i) we have learnt about parity bits.
- (ii) we have learnt how to check error of a message using even or odd parity.
- (iii) we learnt how to design a parity bit checker circuit.
- (iv) we have also learnt how to convert BCD code to Excess-3 code.
- (v) we have also learnt how to implement code converter using basic gates.

**THE END**